

## **Table of Contents:**

<b>Introduction</b>	<b>2</b>
<b>Components:</b>	
Latch 1	<b>2</b>
Latch 2	<b>3</b>
4:16 Decoder	<b>4</b>
Finite State Machine	<b>6</b>
<b>Problem 1</b>	<b>11</b>
<b>Problem 2 Selection B)</b>	<b>16</b>
<b>Problem 3 Selection B)</b>	<b>23</b>
<b>Conclusion</b>	<b>26</b>

## **Introduction:**

The lab “Design of a Simple General Purpose Processor” covers all the concepts and ideas studied contained in this course, ranging from Seven segment display, Decoder, and Finite State machine (FSM) which were all taught and tested in previous labs. The main purpose of this lab is to design and implement an Arithmetic Logic Unit (ALU) that has the ability to perform a multitude of operations, such as logical and arithmetic operations. Which should be able to be displayed on the FPGA board. The other components that are designed and implemented to generate the inputs and produce the outputs for the ALU. The components are the FSM and Decoder which are the control unit, the Latch which is the storage unit, and the Seven segment display which is on the board and is the display.

## **Components:**

### **Latch 1:**

In this experiment, the latches were employed as temporary storage units. This implies latch 1 would temporarily hold input A, which was the final three digits of my student ID. In this instance,  $A(72)_{16} = (0111\ 0010)_2$ . It accepts an 8-bit binary number as input and reads the values on the rising edge of the clock as output on the next rising edge of the clock signal. These outputs are then sent into the ALU component as inputs.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4  ENTITY latch1 IS
5  PORT (A : IN STD_LOGIC_VECTOR(7 DOWNTO 0 );
6        resetn, clock: IN STD_LOGIC;
7        Q1: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
8  END latch1;
9
10 ARCHITECTURE Behavior OF latch1 IS
11 BEGIN
12   Process(resetn, Clock)
13   BEGIN
14     IF resetn = '0' THEN
15       Q1 <= "00000000";
16     ELSIF CLOCK'EVENT AND Clock = '1' THEN
17       Q1 <= A;
18     END IF;
19   END PROCESS;
20 END Behavior;
21
22

```

Figure 1: The VHDL Code for Latch 1

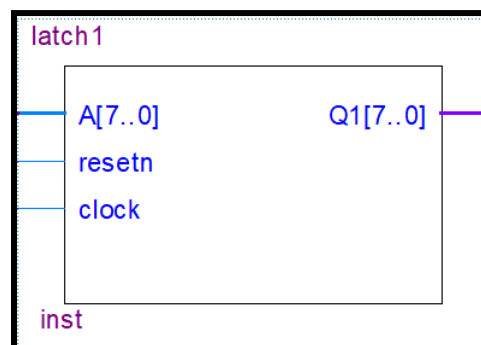


Figure 2: Latch 1 BDF

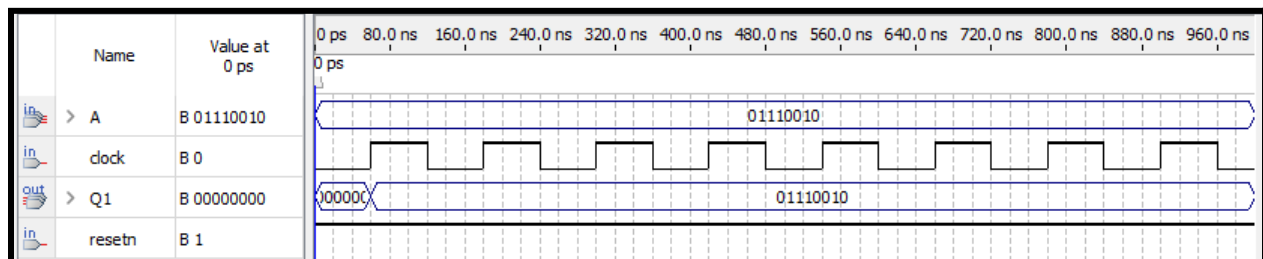


Figure 3: Waveform for Latch(Input A)

## Latch 2:

Latch 2 is designed in the same manner as Latch 1, except it will be used to temporarily store input B. This input will be the binary translation of the final two of the student number's last four digits (i.e.  $B = (12)_{16} = (0001\ 0010)_2$ ). The resulting output will once again be transported into the ALU component.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4  ENTITY latch2 IS
5  PORT (B : IN STD_LOGIC_VECTOR(7 DOWNTO 0 );
6        resetn, clock: IN STD_LOGIC;
7        Q2: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
8  END latch2;
9
10 ARCHITECTURE Behavior OF latch2 IS
11 BEGIN
12   Process(resetn, Clock)
13   BEGIN
14     IF resetn = '0' THEN
15       Q2 <= "00000000";
16     ELSIF CLOCK'EVENT AND Clock = '1' THEN
17       Q2 <= B;
18     END IF;
19   END PROCESS;
20 END Behavior;

```

Figure 4: VHDL Code for Latch 2

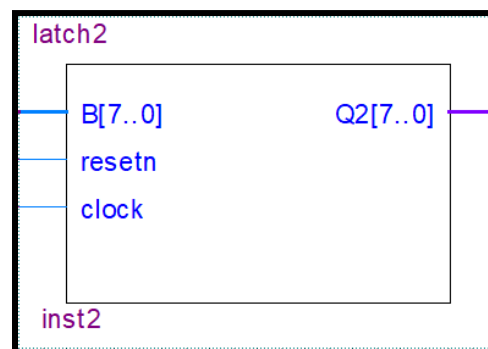


Figure 5: Latch 2 BDF

 


Figure 6: Waveform for Latch(Input B)

## 4:16 Decoder:

One of the two components that comprise the control unit is the 4:16 Decoder. Its goal is to take a 4-bit input and process it to get a 16-bit result. For the purposes of this lab, the 4:16 Decoder will accept a 4-bit value from the FSM and produce microcode, which will then be sent to the ALU. This microcode is critical in selecting which operation the ALU performs.

w3	w2	w1	w0	y15	y14	y13	y12	y11	y10	y9	y8	y7	y6	y5	y4	y3	y2	y1	y0
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0
0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

**Table 1:** Truth Table for 4:16 Decoder

```

1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;
3  ENTITY decod IS
4  PORT ( w : IN STD_LOGIC_VECTOR(3 DOWNTO 0) ;
5        En : IN STD_LOGIC ;
6        y : OUT STD_LOGIC_VECTOR(15 DOWNTO 0) ) ;
7
8  END decod ;
9  ARCHITECTURE Behavior OF decod IS
10     SIGNAL Enw : STD_LOGIC_VECTOR(4 DOWNTO 0) ;
11     BEGIN
12         Enw <= En & w ;
13         WITH w SELECT
14         y <= "1000000000000000" WHEN NOT "0000",
15              "0100000000000000" WHEN NOT "0001",
16              "0010000000000000" WHEN NOT "0010",
17              "0001000000000000" WHEN NOT "0011",
18              "0000100000000000" WHEN NOT "0100",
19              "0000010000000000" WHEN NOT "0101",
20              "0000001000000000" WHEN NOT "0110",
21              "0000000100000000" WHEN NOT "0111",
22              "0000000010000000" WHEN NOT "1000",
23              "0000000001000000" WHEN NOT "1001",
24              "0000000000100000" WHEN NOT "1010",
25              "0000000000010000" WHEN NOT "1011",
26              "0000000000001000" WHEN NOT "1100",
27              "0000000000000100" WHEN NOT "1101",
28              "0000000000000010" WHEN NOT "1110",
29              "0000000000000001" WHEN NOT "1111",
30              "0000000000000000" WHEN OTHERS;
31
32     END Behavior;

```

Figure 7: VHDL Code for 4:16 Decoder


 


Figure 8: 4:16 Decoder BDF

 

**Figure 9: Waveform for 4:16 Decoder**


## Finite State Machine(FSM):

The finite state machine runs through 9 states in a row, beginning with 0 and ending with 8. The code includes the student number, and the only inputs are data in, clock, and reset. For the FSM to work properly, reset is set to 0 and data in is set to 1. Each digit of the student number corresponds to a different state, which changes during the clock cycle. The current state is a 4-bit number that is sent to the 4:16 decoder.

		Current State				Next State			
Student ID	State	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>3</sub>	Q <sub>3</sub>	Q <sub>3</sub>	Q <sub>3</sub>
5	0	0	0	0	0	0	0	0	1
0	1	0	0	0	1	0	0	1	0
1	2	0	0	1	0	0	0	1	1

1	3	0	0	1	1	0	1	0	0
6	4	0	1	0	0	0	1	0	1
7	5	0	1	0	1	0	1	1	0
2	6	0	1	1	0	0	1	1	1
1	7	0	1	1	1	1	0	0	0
2	8	1	0	0	0	0	0	0	0

**Table 2:** Truth Table for FSM

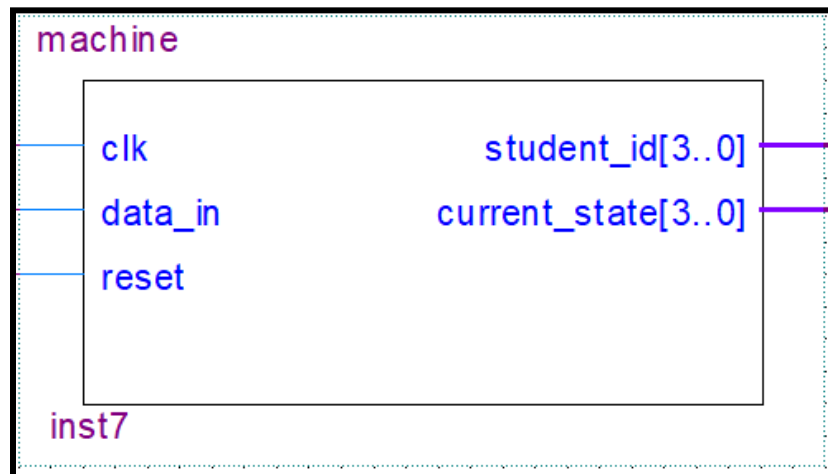

**Figure 10:** Block Diagram for FSM



```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  entity machine is
4      port
5      (
6          clk : in std_logic;
7          data_in : in std_logic;
8          reset : in std_logic;
9          student_id : out std_logic_vector(3 downto 0);
10         current_state: out std_logic_vector (3 downto 0)
11     );
12 end entity;
13
14 architecture fsm of machine is
15
16     type state_type is (s0, s1, s2, s3, s4, s5, s6, s7, s8);
17
18     signal yfsm : state_type;
19
20 begin
21     process(clk, reset)
22     begin
23         if reset = '1' then
24             yfsm <= s0;
25         elsif (clk'EVENT AND clk = '1') then
26
27             case yfsm is
28                 when s0 =>
29                     IF (data_in = '0') then
30                         yfsm <= s0;
31                     ELSE
32                         yfsm <= s1;
33                     END IF;
34                 when s1 =>
35                     IF (data_in = '0') then
36                         yfsm <= s1;
37                     ELSE
38                         yfsm <= s2;
39                     END IF;
40                 when s2 =>
41                     IF (data_in = '0') then
42                         yfsm <= s2;
43                     ELSE
44                         yfsm <= s3;
45                     END IF;
46                 when s3 =>

```

Figure 11: VHDL Code for FSM (Part 1)

```

46         when s3 =>
47             IF (data_in = '0') then
48                 yfsm <= s3;
49             ELSE
50                 yfsm <= s4;
51             END IF;
52         when s4 =>
53             IF (data_in = '0') then
54                 yfsm <= s4;
55             ELSE
56                 yfsm <= s5;
57             END IF;
58         when s5 =>
59             IF (data_in = '0') then
60                 yfsm <= s5;
61             ELSE
62                 yfsm <= s6;
63             END IF;
64         when s6 =>
65             IF (data_in = '0') then
66                 yfsm <= s6;
67             ELSE
68                 yfsm <= s7;
69             END IF;
70         when s7 =>
71             IF (data_in = '0') then
72                 yfsm <= s7;
73             ELSE
74                 yfsm <= s8;
75             END IF;
76         when s8 =>
77             IF (data_in = '0') then
78                 yfsm <= s8;
79             ELSE
80                 yfsm <= s0;
81             END IF;
82         END CASE;
83     END IF;
84 END process;
85
86 process (yfsm, data_in)
87 begin
88     case yfsm is
89         when s0 =>
90             student_id <= "0101";--s#:5
91             current_state <= "0000";

```


Figure 12: VHDL Code for FSM (Part 2)

```

92         when s1 =>
93             student_id <= "0000";--s#:0
94             current_state <= "0001";
95         when s2 =>
96             student_id <= "0001";--s#:1
97             current_state <= "0010";
98         when s3 =>
99             student_id <= "0001";--s#:1
100            current_state <= "0011";
101         when s4 =>
102             student_id <= "0110";--s#:6
103             current_state <= "0100";
104         when s5 =>
105             student_id <= "0111";--s#:7
106             current_state <= "0101";
107         when s6 =>
108             student_id <= "0010";--s#:2
109             current_state <= "0110";
110         when s7 =>
111             student_id <= "0001";--s#:1
112             current_state <= "0111";
113         when s8 =>
114             student_id <= "0010";--s#:2
115             current_state <= "1000";
116     END CASE;
117 END process;
118 END fsm;

```

**Figure 13: VHDL Code for FSM (Part 3)**

 


**Figure 14: Waveform for FSM**

### Problem 1;ALU 1:

The ALU, which is the primary component, is used to carry out the operations. There are five inputs: the Student ID number, OP, the A and B values, and the clock. The FSM output provides the student ID, the decoder output provides the OP, and the latches provide the A and B values. The clock is used to transition between functions. The OP has a 16-bit value that comes from the decoder and is used as microcode to tell the ALU what state it is in. Each state, represented by the 16-bit microcode, has a specific purpose.

Function #	Microcode	Operation / Function
1	0000000000000001	Sum(A, B)
2	0000000000000010	Diff(A, B)
3	0000000000000100	$\overline{A}$
4	0000000000001000	$\overline{A \cdot B}$
5	0000000000010000	$\overline{A + B}$
6	0000000000100000	$A \cdot B$
7	0000000001000000	$A \oplus B$
8	0000000010000000	$A + B$
9	0000000100000000	$\overline{A \oplus B}$

**Table 3:** ALU Operations for Problem Set 1

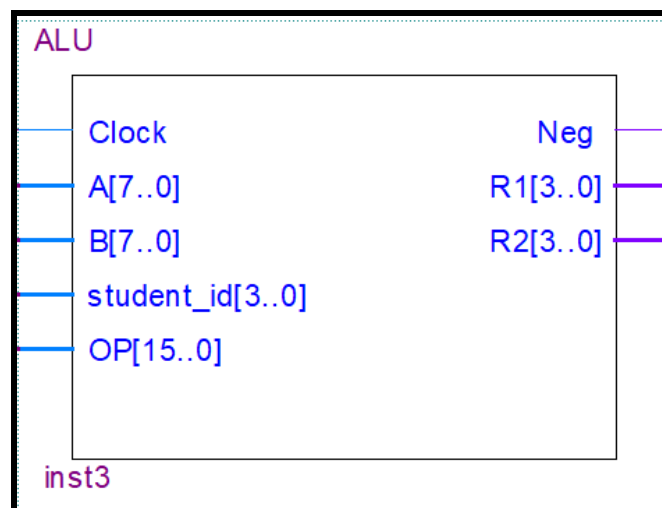

**Figure 15:** The Block Diagram for ALU 1

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  use ieee.numeric_std.all;
5
6  entity ALU is
7  port(Clock      : in std_logic; --input clock signal
8      A,B         : in unsigned (7 downto 0); -- 8 bit inputs from latches A and B
9      student_id  : in unsigned(3 downto 0); --4 bit student id from FSM
10     OP          : in unsigned (15 downto 0); --16 bit selector for Operation from Decoder
11     Neg         : out std_logic;
12     R1          : out unsigned (3 downto 0);
13     R2          : out unsigned (3 downto 0));
14 end ALU;
15
16 architecture calculation of ALU is
17     signal Reg1,Reg2,Result : unsigned(7 downto 0) := (others => '0');
18     signal Reg4 : unsigned(0 to 7);
19 begin
20     Reg1 <= A;--temp variables to do your operations/signal
21     Reg2 <= B;
22     process(Clock, OP)
23     Begin
24         if(rising_edge(Clock)) THEN
25             neg <= '0';
26             case OP is
27                 When "0000000000000001" =>
28                     -- Do Addition for Reg1 and Reg2
29                     result <= A + B;
30
31                 When "0000000000000010" =>
32                     -- Do subtraction
33                     -- Neg bit set if required
34                     if (A < B) then
35                         neg <= '1';
36                         result <= B - A;
37                     else
38                         result <= A - B;
39                     end if;
40
41                 When "0000000000000100" =>
42                     -- do inverse
43                     result <= NOT A;
44
45                 When "0000000000001000" =>
46                     -- do boolean nand

```

**Figure16 :** ALU code for Problem(Part 1)

```

47      result <= NOT (A and B);
48
49      When "0000000000010000" =>
50      -- do boolean Nor
51      result <= NOT (A OR B);
52
53      When "0000000000100000" =>
54      -- do boolean AND
55      result <= A AND B;
56
57      When "0000000001000000" =>
58      -- do boolean xor
59      result <= (A AND (NOT B)) OR ((NOT A) AND B);
60
61      When "0000000010000000" =>
62      -- do boolean or
63      result <= A OR B;
64
65      When "0000000100000000" =>
66      -- do boolean Xnor
67      result <= NOT((A AND (NOT B)) OR ((NOT A) AND B));
68
69      When others =>
70      -- Dont care, do nothing
71
72      end case;
73      end if;
74      end process;
75      R1 <= Result(3 downto 0);
76      R2 <= Result(7 downto 4);
77      end calculation;
78
79
80

```

Figure 17 : ALU code for Problem(Part 2)


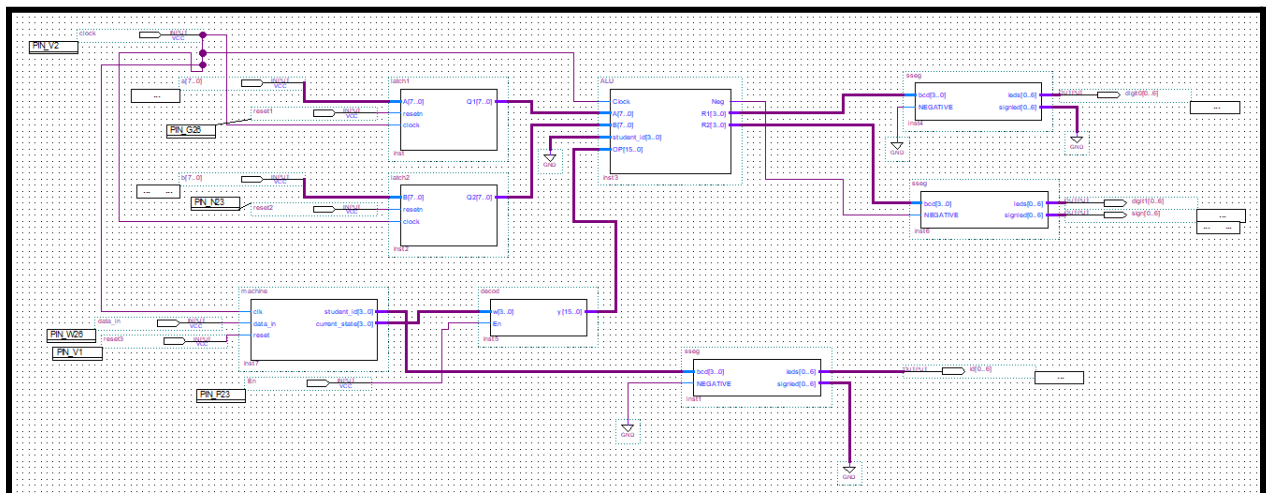


Figure 18: The Block Diagram for Problem 1

 

**Figure 19: Waveform for Problem 1**

According to Figure 19, the first output is "0000," which is not a result of the predicted microcode based on the procedures. This is because there is a delay in the result between the decoder and the ALU. The ALU performs operations on the rising edge of the clock, but the decoder does not. This happens because the ALU performs the operation depending on the FSM's previous state. This is the reason for the "0000" output at the start, as the FSM has no states prior to 0, resulting in the output. This latency is present in ALU 2 and ALU 3.

# Hand Computations for Problem 1:

Problem # 1:  $A: (01110010)_2 = (72)_{16}$   
 $B: (00010010)_2 = (12)_{16}$

Function # 1:  $Sym(A, B)$

$$\begin{array}{r} 01110010 \\ 00010010 \\ \hline 11100101 \end{array} \Rightarrow (84)_{16}$$

Function # 2:  $diff(A, B)$

$$\begin{array}{r} 01110010 \\ -00010010 \\ \hline 01100000 \end{array} \Rightarrow (60)_{16}$$

Function # 3:  $\bar{A}$

$$01110010 \Rightarrow 10001101 \Rightarrow (8D)_{16}$$

$\uparrow$   
not

Function # 4:  $\overline{A \cdot B}$

$$\begin{array}{r} 01110010 \\ 00010010 \\ \hline 11101101 \end{array} \Rightarrow (ED)_{16}$$

Function # 5:  $\overline{A + B}$

$$\begin{array}{r} 01110010 \\ 00010010 \\ \hline 10001101 \end{array} \Rightarrow (8D)_{16}$$

Function # 6:  $A \cdot B$

$$\begin{array}{r} 01110010 \\ 00010010 \\ \hline 00010010 \end{array} \Rightarrow (12)_{16}$$

Function # 7:  $A \oplus B$

$$\begin{array}{r} 01110010 \\ 00010010 \\ \hline 01100000 \end{array} \Rightarrow (20)_{16}$$

$$\begin{array}{r} 5 \\ 0 \\ | \\ 6 \\ 7 \text{ } - 0111 \\ 2 \text{ } - 0010 \end{array} \Bigg\} A$$

$$\begin{array}{r} 1 \text{ } - 0001 \\ 2 \text{ } - 0010 \end{array} \Bigg\} B$$

Function # 8:  $A + B$  or add

$$\begin{array}{r} 01110010 \\ 00010010 \\ \hline 01110010 \end{array} \Rightarrow (72)_{16}$$

Function # 9:  $\overline{A \oplus B}$

$$\begin{array}{r} 01110010 \\ 00010010 \\ \hline 10011111 \end{array} \Rightarrow (9F)_{16}$$



 


Image 1: Problem 1 outputs for FPGA board


### Problem 2; ALU 2; Selection B):

This ALU functioned similarly to ALU 1. It worked precisely the same manner, with the identical variables and code structure. The only change was that new and different logic functions had to be performed. These functions were described in the lab handbook, and problem set B was assigned to this experiment.

Function #	Microcode	Operation / Function
1	0000000000000001	Swap the lower and upper 4 bits of <b>A</b>
2	0000000000000010	Produce the result of ORing <b>A</b> and <b>B</b>
3	0000000000000100	Decrement <b>B</b> by 5
4	0000000000001000	Invert all bits of <b>A</b>
5	0000000000010000	Invert the bit-significance of <b>A</b>
6	0000000000100000	Find the greater value of <b>A</b> and <b>B</b> and produce the results

		(Max( <b>A</b> , <b>B</b> ))
7	0000000001000000	Produce the difference between <b>A</b> and <b>B</b>
8	0000000001000000	Produce the result of XNORing <b>A</b> and <b>B</b>
9	0000000010000000	Rotate <b>B</b> to the left by three bits (ROL)

**Table 4:** ALU Operations for Problem Set 2

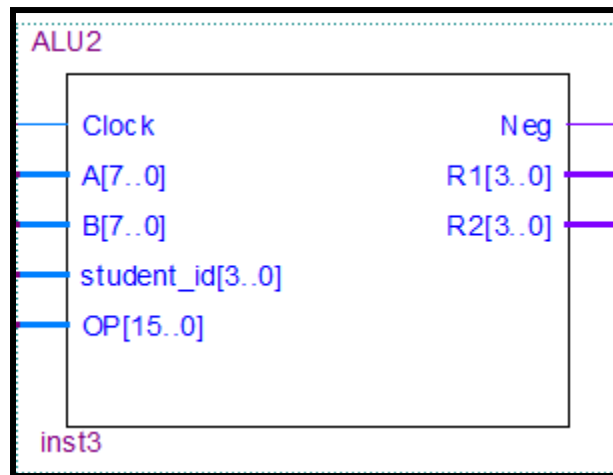

**Figure 20:** Block Diagram for ALU 2

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  use ieee.numeric_std.all;
5
6  entity ALU2 is
7  port(Clock      : in std_logic; --input clock signal
8       A,B        : in unsigned (7 downto 0); -- 8 bit inputs from latches A and B
9       student_id  : in unsigned(3 downto 0); --4 bit student id from FSM
10      OP          : in unsigned (15 downto 0); --16 bit selector for Operation from Decoder
11      Neg         : out std_logic;
12      R1          : out unsigned (3 downto 0);
13      R2          : out unsigned (3 downto 0));
14  end ALU2;
15
16  architecture calculation of ALU2 is
17  signal Reg1,Reg2,Result : unsigned(7 downto 0) := (others => '0');
18  signal Reg4 : unsigned(0 to 7);
19  begin
20  Reg1 <= A;
21  Reg2 <= B;
22  process(Clock, OP)
23  Begin
24      if(rising_edge(Clock)) THEN
25          neg <= '0';
26          case OP is
27              When "0000000000000001" =>
28                  -- Swap the lower and upper 4 bits of A
29                  Result(7 downto 4) <= A(3 downto 0);
30                  Result(3 downto 0) <= A(7 downto 4);
31
32              When "0000000000000010" =>
33                  -- Produce the result of ORing A and B
34                  Result <= A OR B;
35
36              When "0000000000000100" =>
37                  -- Decrement B by 5
38                  Result <= B - 5;
39
40
41              When "0000000000001000" =>
42                  -- Invert all bits of A
43                  Result <= NOT A;
44
45              When "0000000000010000" =>
46                  -- Invert the bit-significance order of A

```


**Figure 21:** ALU Code for Problem 2(Part 1)

```


47   for i in 0 to 7 loop
48       Result(i) <= Reg1(7-i);
49   end loop;
50   Neg <= '0';
51
52   When "00000000001000000" =>
53       -- Find the greater value of A and B and produce the results
54   if(A > B) THEN
55       Result <= A;
56   else
57       Result <= B;
58   end if;
59
60   When "00000000010000000" =>
61       -- Produce the difference between A and B
62   if (A < B) then
63       Result <= B - A;
64   else
65       Result <= A - B;
66   end if;
67
68   When "00000000100000000" =>
69       -- Produce the result of XNORING A and B
70   Result <= NOT((A AND (NOT B)) OR ((NOT A) AND B));
71
72   When "00000001000000000" =>
73       -- Rotate B to the left by three bits(ROL)
74   Result <= (B rol 3);
75
76   When others =>
77       -- Dont care, do nothing
78
79   end case;
80   end if;
81   end process;
82   R1 <= Result(3 downto 0);
83   R2 <= Result(7 downto 4);
84   end calculation;

```

**Figure 22:**ALU Code for Problem 2 (Part 2)

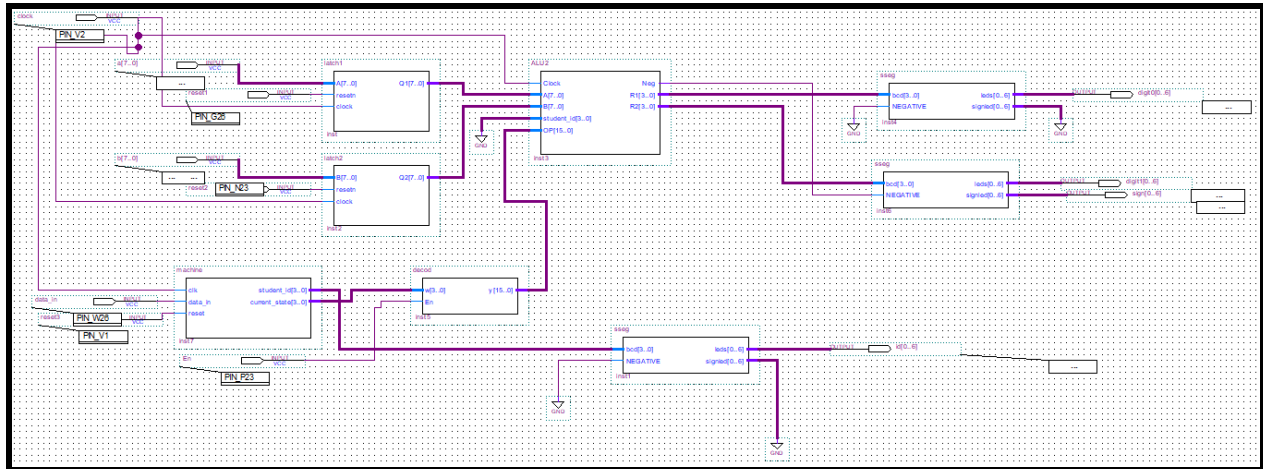

**Figure 23:** Block Diagram for Problem 2

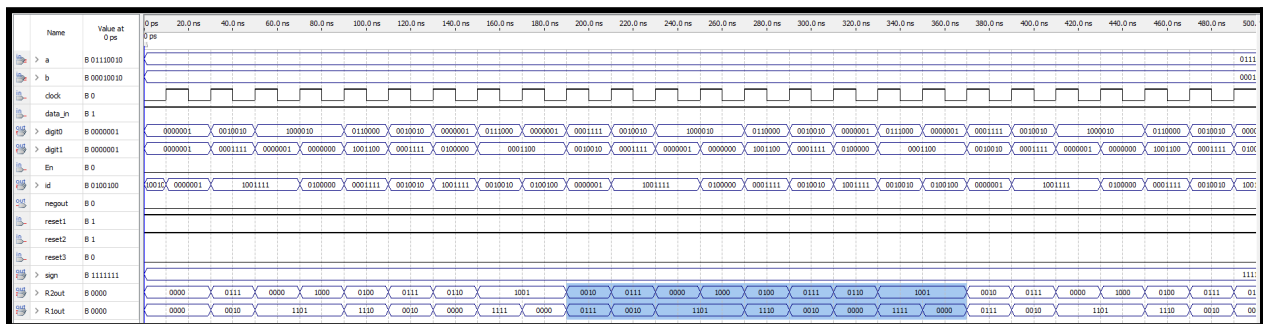

**Figure 24: Waveform for Problem 2**

According to Figure 19, the first output is "0000," which is not a result of the predicted microcode based on the procedures. This is because there is a delay in the result between the decoder and the ALU. The ALU performs operations on the rising edge of the clock, but the decoder does not. This happens because the ALU performs the operation depending on the FSM's previous state. This is the reason for the "0000" output at the start, as the FSM has no states prior to 0, resulting in the output. As explained in Problem 1, the student number and the operations are not synchronized.

## Hand Computations for Problem 2:

Problem #2

$$A: (01110010)_2 = (72)_{10}$$

$$B: (00010010)_2 = (12)_{10}$$

Function #1: Swap the Lower and upper 4 bits of A

$$A = 01110010 \rightarrow 00101110 = (27)_{10}$$

Function #2: Produce the result of ORing A and B

$$\begin{array}{r} 01110010 \\ 00010010 \\ \hline 01110010 \end{array} = (72)_{10}$$

Function #3: Decrement B by 5

$$\begin{array}{r} 00010010 \\ -00000101 \\ \hline 00001101 \end{array} \Rightarrow (9)_{10}$$

Function #4: Invert all bits of A

$$\bar{A} = 01110010 \Rightarrow 10001101 = (85)_{10}$$

Function #5: Invert all bit-significance of A

$$A = 01110010 \Rightarrow (10001101)_2 = (85)_{10}$$

Function #6: Find the greater value of A and B and produce the result  $(\max(A, B))$

$$A = 01110010 > B = 00010010$$

$$\max(A, B) = (01110010)_2 = (72)_{10}$$

Function #7: Produce the difference between A and B

$$\begin{array}{r} 01110010 \\ -00010010 \\ \hline 01100000 \end{array} \Rightarrow (60)_{10}$$


Function #8: Produce the result of XORing A and B

$$\begin{array}{r} 01110010 \\ 00010010 \\ \hline 01100000 \end{array} = (96)_{10}$$

Function #9: Rotate B to Left by three bits (ROL)
 
$$B = 00010010 \Rightarrow (10010000)_2 = (90)_{10}$$

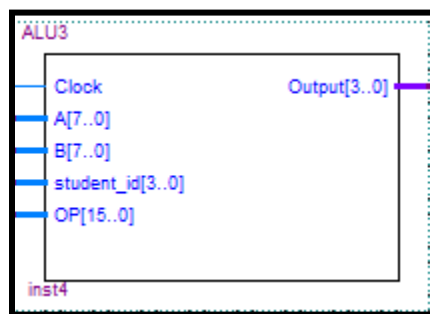




**Image 2:** Problem 2 outputs for FPGA board

### Problem 3 ;ALU 3; Selection B):

This ALU worked in a different way than the preceding ones. This is because it is much simpler to operate because it has fewer functions to perform. For this section, problem set B was assigned once again. ALU 3 had to determine whether the digits of the student number were even or odd. The code will set the output variable "result" to "0000" if it is even, and "0001" if it is odd. This output was then fed into a modified SSEG. This new SSEG will output a "y" on the FPGA board if the input value is "0000" and a "n" if the input value is "0001".



**Figure 25:** Symbol Block for ALU 3



```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  use ieee.numeric_std.all;
5
6  entity ALU3 is
7  port(Clock      : in std_logic; --input clock signal
8       A,B        : in unsigned (7 downto 0); -- 8 bit inputs from latches A and B
9       student_id  : in unsigned(3 downto 0); --4 bit student id from FSM
10      OP          : in unsigned (15 downto 0); --16 bit selector for Operation from Decoder
11      Output       : out unsigned(3 downto 0));
12  end ALU3;
13
14  architecture calculation of ALU3 is
15  signal Result : unsigned(3 downto 0) := (others => '0');
16  signal Reg4 : unsigned(0 to 7);
17  begin
18
19  process(Clock, OP)
20  Begin
21      if(rising_edge(Clock)) THEN
22      case OP is
23          When "0000000000000001" =>
24              --Even
25              if (student_id mod 2) = 0 then
26                  result <= "1111";
27              --Odd
28              else
29                  result <= "0000";
30              end if;
31
32          When "0000000000000010" =>
33              --Even
34              --Even
35              if (student_id mod 2) = 0 then
36                  result <= "1111";
37              --Odd
38              else
39                  result <= "0000";
40              end if;
41
42          When "0000000000000100" =>
43              --Even
44              if (student_id mod 2) = 0 then
45                  result <= "1111";
46              --Odd

```

Figure 26:ALU Code for problem 3(part 1)

```

47      else
48      result <= "0000";
49      end if;
50
51      When "000000000000010000" =>
52      --Even
53      if (student_id mod 2) = 0 then
54      result <= "1111";
55      --Odd
56      else
57      result <= "0000";
58      end if;
59
60
61      When "000000000000100000" =>
62      --Even
63      if (student_id mod 2) = 0 then
64      result <= "1111";
65      --Odd
66      else
67      result <= "0000";
68      end if;
69
70      When "000000000001000000" =>
71      --Even
72      if (student_id mod 2) = 0 then
73      result <= "1111";
74      --Odd
75      else
76      result <= "0000";
77      end if;
78
79      When "000000000010000000" =>
80      --Even
81      if (student_id mod 2) = 0 then
82      result <= "1111";
83      --Odd
84      else
85      result <= "0000";
86      end if;
87
88      When "000000000100000000" =>
89      --Even
90      if (student_id mod 2) = 0 then
91      result <= "1111";
92      --Odd

```


**Figure 27: ALU Code for problem 3(part 2)**

```

94      result <= "0000";
95      end if;
96
97      When "000000001000000000" =>
98      --Even
99      if (student_id mod 2) = 0 then
100      result <= "1111";
101      --Odd
102      else
103      result <= "0000";
104      end if;
105
106
107      When others =>
108      -- Dont care, do nothing
109
110      end case;
111      end if;
112      end process;
113      Output <= result(3 downto 0);
114      end calculation;
115


```

**Figure 28:**ALU Code for problem 3(part 3)

 


**Figure 29:** Symbol Block for Modified Seven Segment Display
 
### Figure 30: Code for Modified Seven Segment Display



The student number and the operations are not synced, as indicated in Problem 1. The procedure that shows 'y' for even numerals and 'n' for odd digits is not synchronized in the figures below. It shows the outcome for the preceding student digit.

 

**Image 2:** Problem 2 outputs for FPGA board

## Conclusion:

The primary goal of this lab was to develop and create an ALU component in the VHDL environment that performed varied operations based on the state, inputs, and written code. This task was accurately completed as a General-Purpose Processor (GPP) was designed, implemented, compiled, and tested. The GPP was a combination of control and storage units, Arithmetic and logic units, and the Seven segment display. The general purpose processor was built on the FPGA board once all of the code was written and compiled. Handwritten solutions were compared to device data to check that the lab was completed correctly. After assembling these components, the implementation into the FPGA board was successful.